
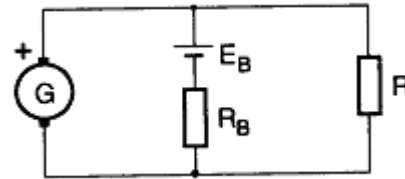


opgave 2.42

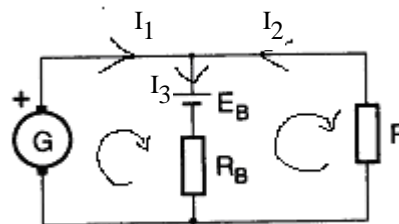

$$E_{\text{generator}} := 27 \cdot \text{V} \quad E_{\text{batteri}} := 24 \cdot \text{V}$$

$$R_{\text{generator}} := 1 \cdot \Omega \quad R_{\text{batteri}} := 2 \cdot \Omega \quad R_{\text{belastning}} := 8 \cdot \Omega$$




$$I_3 = I_1 + I_2$$

$$E_{\text{generator}} - E_{\text{batteri}} = I_1 \cdot R_{\text{generator}} + I_3 \cdot R_{\text{batteri}}$$

$$E_{\text{batteri}} = -I_3 \cdot R_{\text{batteri}} - I_2 \cdot R_{\text{belastning}}$$

$$\left(\begin{array}{l} I_3 = I_1 + I_2 \\ E_{\text{generator}} - E_{\text{batteri}} = I_1 \cdot R_{\text{generator}} + I_3 \cdot R_{\text{batteri}} \\ E_{\text{batteri}} = -I_3 \cdot R_{\text{batteri}} - I_2 \cdot R_{\text{belastning}} \end{array} \right) \text{solve}, I_1, I_2, I_3 \rightarrow \left(\begin{array}{ccc} \frac{3 \cdot \text{V}}{\Omega} & -\frac{3 \cdot \text{V}}{\Omega} & 0 \end{array} \right) = (3 \quad -3 \quad 0) \text{ A}$$

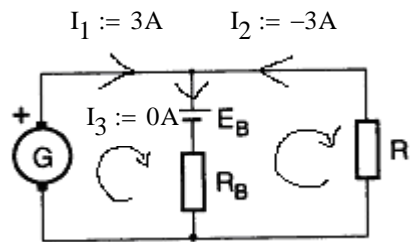

$$U_{klg} := E_{\text{generator}} - I_1 \cdot R_{\text{generator}} = 24 \text{ V}$$

$$U_{klb} := E_{\text{batteri}} - I_3 \cdot R_{\text{batter}} \rightarrow 24 \cdot \text{V}$$

$$U_{kl} := -I_2 \cdot R_{\text{belastning}} \rightarrow 24 \cdot \text{A} \cdot \Omega$$