

6.31

En spole har en resistans  $R := 2\Omega$  og en induktans  $L := 20\text{mH}$

Spolen tilsluttes  $U := 110\text{V}$ ,  $f := 50\text{Hz}$

Beregn

- a) spolens reaktans
- b) spolens impedans
- c) strømstyrken.

a) spolens reaktans

$$X_L := 2\pi \cdot f \cdot L$$

$$X_L = 6.283 \Omega$$

b) spolens impedans

$$Z := \sqrt{R^2 + X_L^2}$$


$$Z = 6.594 \Omega$$

c) strømstyrken.

$$I := \frac{U}{Z}$$

$$I = 16.682 \text{ A}$$



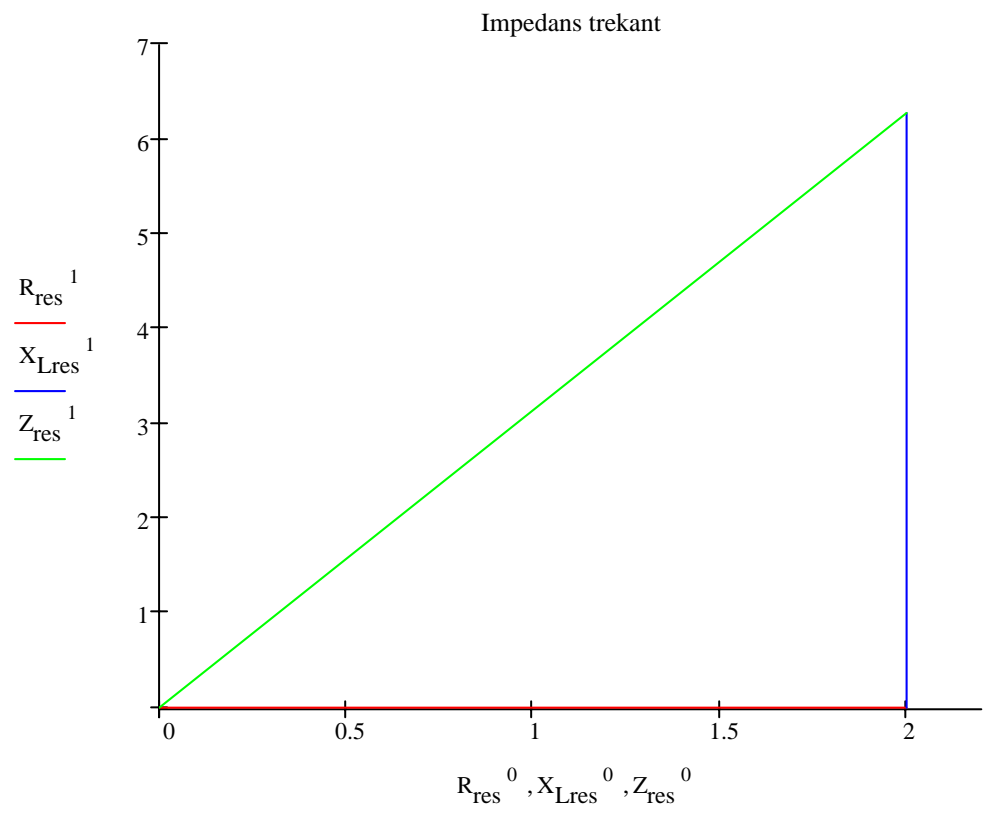

kompleks:

$$L_{\text{kom}} := 20\text{mH}$$

$$X_{L\text{kom}} := 2\pi \cdot f \cdot L_{\text{kom}}$$

$$X_{L\text{kom}} = 6.283i \Omega$$

$$Z_{\text{kom}} := R + X_{L\text{kom}}$$

$$Z_{\text{kom}} = 2 + 6.283i \Omega$$

$$|Z_{\text{kom}}| = 6.594 \Omega$$

$$\arg(Z_{\text{kom}}) = 72.343 \text{ deg}$$

$$I_{\text{kom}} := \frac{U}{Z_{\text{kom}}}$$

$$I_{\text{kom}} = 5.06 - 15.896i \text{ A}$$

$$|I_{\text{kom}}| = 16.682 \text{ A}$$

$$\arg(I_{\text{kom}}) = -72.343 \text{ deg}$$